 


# A Locality-Preserving One-Sided Binary Tree – Crossbar Switch Wiring Design Algorithm


---

Devrim Şahin  
Bilkent University

# INTRODUCTION



$X \rightarrow Y$

 


$X \rightarrow X$

One-sided switches make connections from a set  $X$  onto itself, instead of another set  $Y$

A complete one-sided switch can be represented by a  $K_n$  graph

# ONE-SIDED SWITCH

 


This is an implementation of a one-sided crossbar switch

Each  $x_i$  has a permanent connection to each  $x_j$  ( $i \neq j$ )

Each connection can be used by closing two elementary switches

**Problem:** Each terminal has a fanout of  $(n-1)$
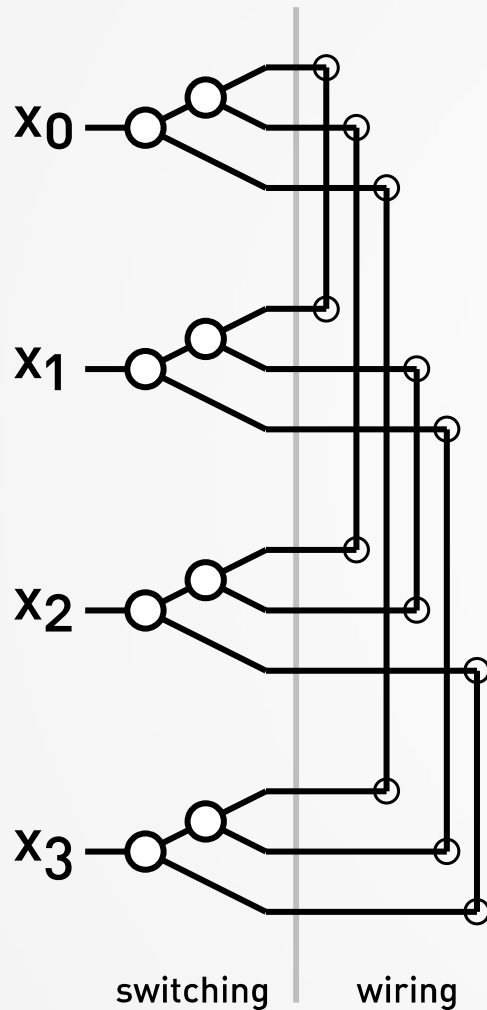
# ONE-SIDED BINARY TREE – CROSSBAR SWITCH



**Solution:** Using binary trees

Each terminal effectively has a fanout of 2

Each binary tree will have a depth of  $\lceil \log_2(n-1) \rceil$


**Problem:** Wiring section has rather long connections

**Solution:** Reordering 'rows'

Rows (horizontal wires) are ordered as:

$(x_0, x_0, x_0)$ ,  $(x_1, x_1, x_1)$ ,  $(x_2, x_2, x_2)$ ,  $(x_3, x_3, x_3)$
 
# ONE-SIDED BINARY TREE – CROSSBAR SWITCH



We can re-order rows to be:


$(x_0, x_1, x_2, x_3), (x_0, x_1, x_2, x_3), (x_0, x_1, x_2, x_3)$

This simplifies the wiring section greatly

In fact, we know that when ordered such, there exists a wiring scheme where the total number of columns in the wiring section does not exceed  $\lfloor n/2 \rfloor$  (Proof)

**Problem:** Switching side became complicated
 
# IMPLEMENTING THE SWITCHING STEP ON A GRID



A simple implementation of the switching step (wiring part is hidden)

Previously, we claimed that there exists a wiring scheme with at most  $\lfloor n/2 \rfloor$  columns. We propose a method to actually design that scheme.

# DESIGNING A WIRING SCHEME

One method appeals to cyclic permutation groups

For our example, cyclic permutation groups are:

$$p = (0123), \quad p^2 = (02)(13), \quad p^3 = (0321)$$




To obtain a wiring scheme, pair the numbers:

$$p = (0123), \quad p^2 = (02)(13), \quad p^3 = (0321)$$

The connections to be made are:

$$(01), (23), (02), (13), (03), (21)$$

Wiring is shown on the right

   

# DESIGNING A WIRING SCHEME

However this method might become tedious for odd  $n$ :

$$p = (01234) \rightarrow (01)(23)(4)$$

$$p^2 = (02413) \rightarrow (02)(41)(3)$$

$$p^3 = (03142) \rightarrow (03)(1)(42)$$

$$p^4 = (04321) \rightarrow (04)(3)(21)$$

Note that (43) and (13) were not generated.

We introduce another intuitive method appealing to adjacency matrices



# ADJACENCY MATRICES

We represent each connection between terminals  $x_i$  and  $x_j$  with the pair  $\langle i, j \rangle$

Since we assume connections are two-way (undirected),  $\langle i, j \rangle = \langle j, i \rangle$


For  $n$  terminals, we can represent all the connections with an  $n \times n$  adjacency matrix  $\mathbf{A}$

Here,  $\mathbf{A}_{i,j}$  corresponds to the pair  $\langle i, j \rangle$

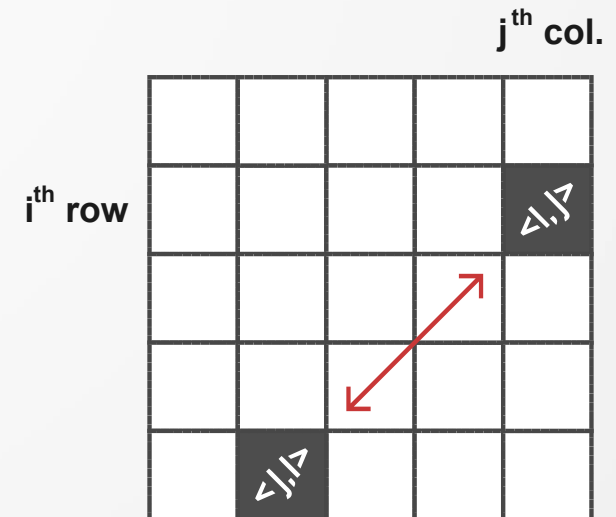**Then  $\mathbf{A}$  is symmetric ( $\mathbf{A}_{i,j} = \mathbf{A}_{j,i}$ )**

For a complete  $K_n$  graph,

all  $\mathbf{A}_{i,j}$  must be 1 ( $i \neq j$ )



# GROUPING PAIRS

To design a complete wiring scheme, we should cover all the upper triangle in the matrix


**Method:** Diagonally scan the matrix

Define pairs of groups as  $\langle x, (x+k) \bmod n \rangle$

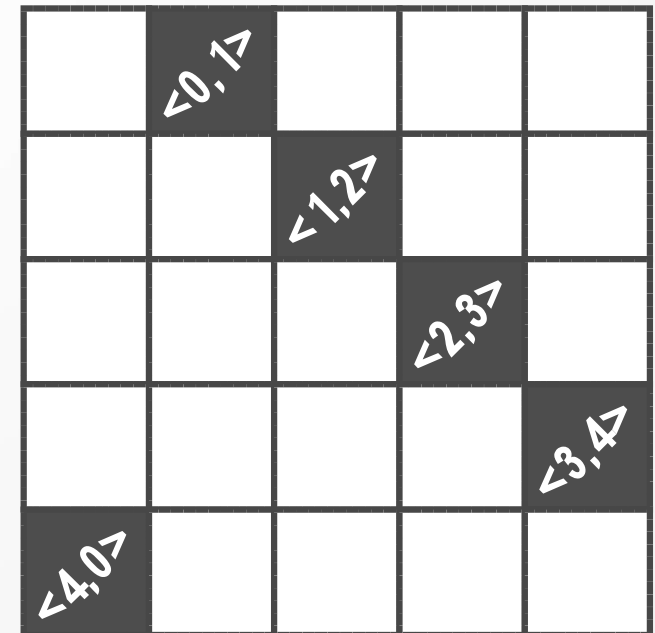**Example:**  $n=5, k=1, 0 \leq x < n$

Pairs are

$\langle 0,1 \rangle, \langle 1,2 \rangle, \langle 2,3 \rangle, \langle 3,4 \rangle, \langle 4,0 \rangle$




# GROUPING PAIRS – ODD $n$ CASE

We should diagonally cover the entire upper triangle by changing  $k$


**Example:**  $n=7$ ,  $k=1,2,3$ ,  $0 \leq x < n$

(All pairs are shown in the upper triangle)


$\langle x, (x+1) \bmod n \rangle$

 

$\langle x, (x+2) \bmod n \rangle$

 

$\langle x, (x+3) \bmod n \rangle$

 

We repeat for all  $k$  in the range  $[1, \text{floor}(n/2)]$


This works well **for odd  $n$**

# GROUPING PAIRS – EVEN $n$ CASE


For even  $n$ , should consider the case  $k=n/2$  separately

**Example:**  $n=8$ ,  $k=1,2,3,4$ ,  $0 \leq x < n$


$\langle x, (x+1) \bmod n \rangle$

 


$\langle x, (x+2) \bmod n \rangle$

 

$\langle x, (x+3) \bmod n \rangle$

 

$\langle x, x+(n/2) \rangle$

 

If we used  $\langle i, (i+k) \bmod n \rangle$  for  $k=n/2$ ; we would cover one diagonal twice

We can solve this special case by changing the range of  $x$  for  $k=n/2$ :

$\langle x, x+n/2 \rangle$   $0 \leq x < n/2$  (instead of  $n$ )

# GROUPING PAIRS – FORMAL DEFINITION

Below are the formal definitions of these two cases:

*For odd n:*

$$\langle x, (x+k) \bmod n \rangle, \quad 0 \leq x < n, \quad 1 \leq k < n/2 \quad (\mathbf{Eqn.1})$$

*For even n:*

$$\langle x, (x+k) \bmod n \rangle, \quad 0 \leq x < n, \quad 1 \leq k < n/2 \quad (\mathbf{Eqn.1})$$

**and**

$$\langle x, x+n/2 \rangle, \quad 0 \leq x < n/2 \quad (\mathbf{Eqn.2})$$

## GROUPING PAIRS – WHY?

What is the advantage of grouping pairs in this fashion?

For each  $k$  in Eqn. 1, we have  $n$  pairs

Each terminal  $x_i$  appears twice in these pairs (*Proof in the paper*):  $\langle i, \bullet \rangle$  and  $\langle \bullet, i \rangle$

To implement all pairs for a given  $k$ , we need exactly two copies of every  $x_i$

There are no interconnections between different  $k$

From the switching section, we can assign two blocks  $(x_0, x_1, \dots, x_{n-1})$  to each  $k$  and wire them independently

# WIRING

Eqn.2 is simple to implement

$$\langle x, x+n/2 \rangle, \quad 0 \leq x < n/2$$


Each  $x_i$  appears **once**, therefore one block is sufficient

**Example:**  $n=8, k=4$

Pairs:  $\langle 0,4 \rangle, \langle 1,5 \rangle, \langle 2,6 \rangle, \langle 3,7 \rangle$



Connections are trivial

Number of columns:  $n/2$  ✓

 
 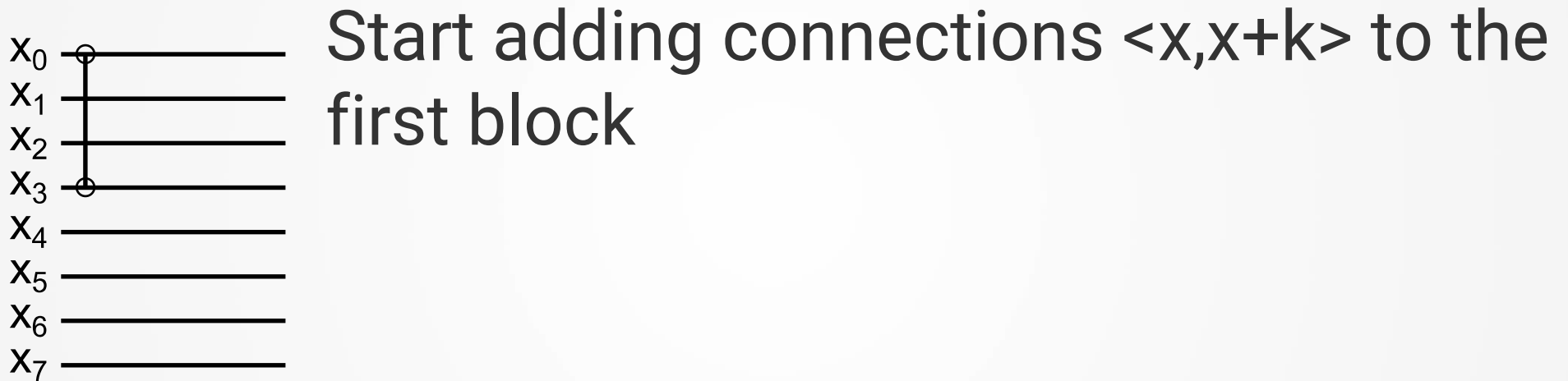
# WIRING


Implementation of Eqn.1 for a given  $k$  over an example:  $n=8, k=3$





 
# WIRING

Implementation of Eqn.1 for a given  $k$  over an example:  $n=8, k=3$





Start adding connections  $\langle x, x+k \rangle$  to the first block

 After adding  $k$  connections,  $\langle k, 2k \rangle$  will collide with  $\langle 0, k \rangle$



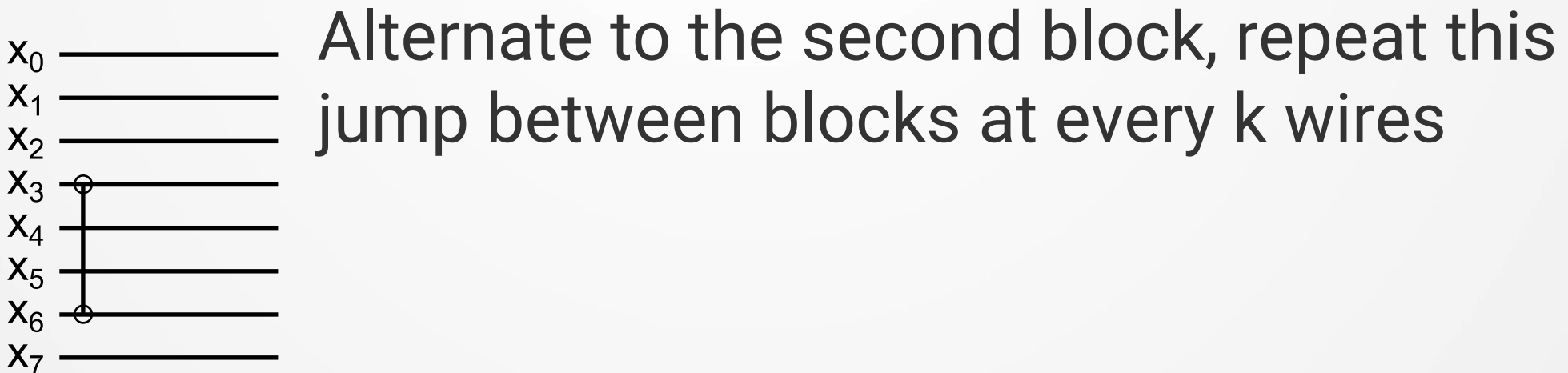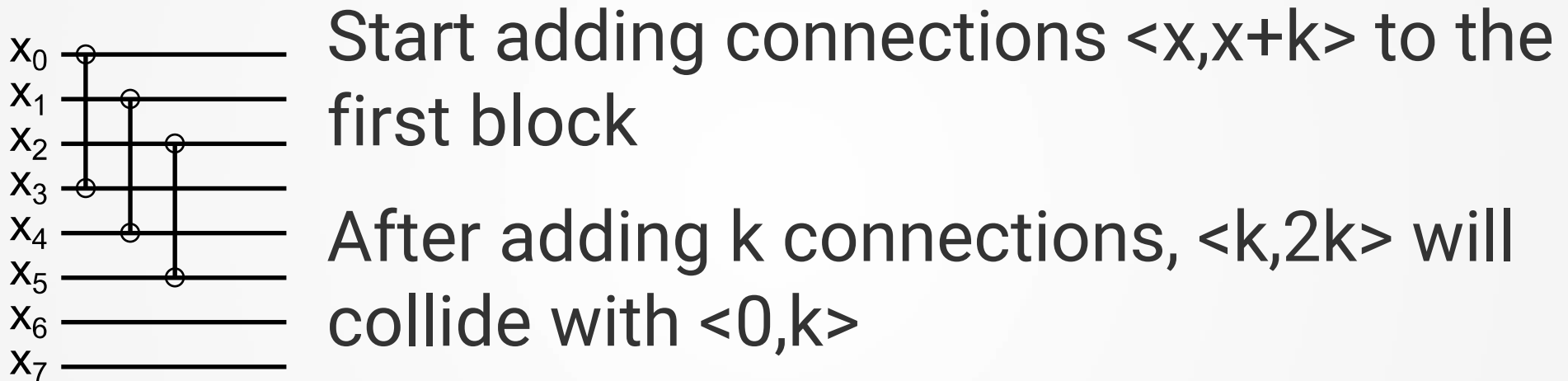
# WIRING

Implementation of Eqn.1 for a given  $k$  over an example:  $n=8$ ,  $k=3$


 
# WIRING


Implementation of Eqn.1 for a given  $k$  over an example:  $n=8, k=3$




Pair  $\langle 5,0 \rangle$  is a 'reverse pair', that is,  $5 > 0$  unlike other pairs due to the modulo operator. For a reverse pair  $\langle i,j \rangle$ , always pick  $j$  from the second block
 
# WIRING

Implementation of Eqn.1 for a given  $k$  over an example:  $n=8, k=3$



 
Pair  $\langle 5,0 \rangle$  is a 'reverse pair', that is,  $5 > 0$  unlike other pairs due to the modulo operator. For a reverse pair  $\langle i,j \rangle$ , always pick  $j$  from the second block



Again, we have added  $k$  connections. Collision happens, alternate to block 1
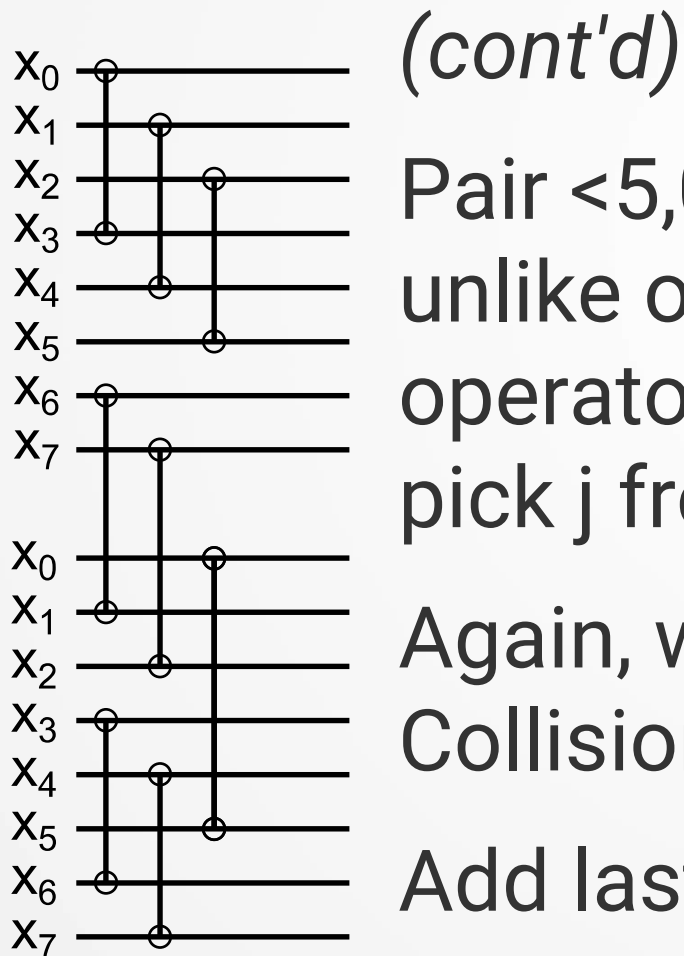
# WIRING

Implementation of Eqn.1 for a given  $k$  over an example:  $n=8, k=3$




Pair  $\langle 5,0 \rangle$  is a 'reverse pair', that is,  $5 > 0$  unlike other pairs due to the modulo operator. For a reverse pair  $\langle i,j \rangle$ , always pick  $j$  from the second block

Again, we have added  $k$  connections. Collision happens, alternate to block 1  
Add last wires and finalize.
 
# WIRING

To obtain complete wiring, repeat for every  $k$ :

(Reverse pairs are shown as aligned right)



Number of columns is bounded by  $\text{floor}(n/2)$

# CONCLUSION

We have introduced a method that constructs a one-sided binary tree – crossbar switch that:

- has at most  $\text{floor}(n/2)$  columns,
- has no connections between pairs of blocks, thus preserving locality,
- is one-pass in nature,
- algorithmically simple.

An implementation can be found at

<https://github.com/kubuzetto/crossbarWiring/>

**THANK YOU FOR YOUR PATIENCE!**

Questions?